

Lecture 12, Oct 18, 2023

Regulator Circuits

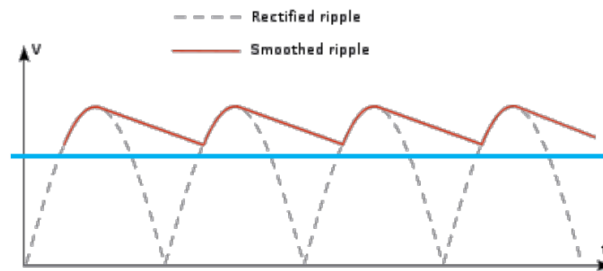


Figure 1: Voltage regulator input vs. output.

- The goal of a regulator is to produce a constant DC output voltage (generally from a higher input voltage) which is constant and steady under load variation
- A regulator is often attached to the output of an AC rectification circuit, which is noisy and contains ripples
- We want the output of our regulator to look like the blue plot above, even if the input voltage varies or if the output load draws varying amounts of current
- Two properties of regulators are of interest:
 - *Line regulation*: holding output constant while input voltage changes
 - * This is usually analyzed under the worst-case load current scenario
 - * For simple regulators, the highest load current is typically the worst-case scenario; for more complex regulators this can be the lowest load current
 - * This is generally quantified as the difference between V_{OUT} at maximum V_{IN} and V_{OUT} at minimum V_{IN} (both at the worst load current), normalized by the design V_{OUT} (nominal value)
 - Note sometimes the V_{OUT} at max or min input voltage are used as normalization for more complex circuits
 - * Line regulation is often expressed as a percentage, which would be the percent change in V_{OUT} for every 1% change in V_{IN}
 - Single digit values are good, double digit values are generally poor
 - *Load regulation*: holding output constant while load current changes
 - * For simple regulators, the lowest input voltage is typically the worst-case scenario
 - * This is generally quantified as the difference between V_{OUT} at minimum load and V_{OUT} at maximum load (both at the worst input voltage), normalized at the V_{OUT} at maximum load
 - Note we are doing min minus max, because generally with a higher load we expect the output voltage to go down
 - Some manufacturers will normalize by V_{OUT} at minimum load or nominal V_{OUT}
 - Load and line regulation are signed quantities, but they are typically positive unless there is feedback in the circuit
- For most simple (no active feedback) regulator circuits, the ends of the input/current draw ranges are usually where the regulator behaves the poorest
- Most regulator circuits take advantage of the fact that the voltage drop across a diode in forward bias is nearly constant
 - Typically if a regulator circuit is working, diodes will be in forward bias mode
- Let's try to design a regulator with the following requirements:
 - Input voltage varies from 10-15V
 - Load current varies from 0-1A
 - Desired output is 9V
- Example: series diode regulator

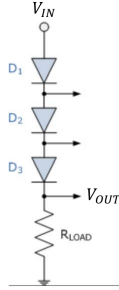


Figure 2: Series diode regulator.

- R_{LOAD} is a placeholder load which can draw varying amounts of current as specified above
- We will be using the piecewise-linear model with $V_{D_0} = 0.5\text{ V}$ and $r_D = 0.1\ \Omega$
- On a high level we expect the output to be a constant voltage offset from the input due to the series diodes
- This regulator has poor line regulation, but good load regulation
- To find line regulation, we solve the circuit for $V_{IN} = 10\text{ V}$ to 15 V ; in both cases we solve with $I_{LOAD} = 1\text{ A}$ since it is our worst-case scenario
 - * Assuming forward bias on all diodes, we have 3 resistors r_D in series and 3 voltage sources V_{D_0} in series
 - * Note generally when diodes are in series with no connections in-between, they will always have the same state
 - * At $V_{IN} = 10\text{ V}$, $I_{LOAD} = 1\text{ A}$ each r_D has a voltage drop of 0.1 V and each V_{D_0} has a voltage drop of 0.5 V , resulting in 8.2 V
 - * At $V_{IN} = 15\text{ V}$, the analysis is similar and we get 13.2 V
 - * The line regulation is then $\frac{13.2 - 8.2}{9} = 55.6\%$, which is very bad
 - * Note for this circuit, it doesn't matter what load current we chose
- To find load regulation, we solve the circuit for $I_{LOAD} = 0\text{ A}$ to $I_{LOAD} = 1\text{ A}$
 - * First assume $V_{IN} = 10\text{ V}$, then at $I_{LOAD} = 0\text{ A}$ we have 8.5 V and at $I_{LOAD} = 1\text{ A}$ we have 8.2 V
 - The load regulation is $\frac{8.5 - 8.2}{8.2} = 3.7\%$ which is pretty good
 - * If we solve at $V_{IN} = 15\text{ V}$, we get 13.5 V at no load and 13.2 V at maximum load
 - The load regulation is $\frac{13.5 - 13.2}{13.2} = 2.3\%$, which is better than the minimum input voltage case
 - This confirms that the minimum input voltage is the worst case